

Impedance Matching

Microwave Seminar

J. Richie

February 22, 2013

Outline

Introduction

Narrow-Band Methods

- Lumped Element Matching
- Stub Tuners
- Quarter-Wave Transformer

Varying Bandwidth Methods

- Lumped Element Methods
- Multiple Quarter-wave Sections
- Bode-Fano Criterion
- Theory of Small Reflections

Conclusions

T-lines, Loads, and Input Impedance

- ▶ Transmission Line Types (many more than listed here)
 - ▶ Coaxial Line
 - ▶ Twin Lead
 - ▶ Microstrip, Stripline, etc.
- ▶ The Load: Z_L
- ▶ Input Impedance:

$$Z_{in} = R_o \frac{Z_L + jR_o \tan \beta \ell}{R_o + jZ_L \tan \beta \ell}$$

Narrow-Band Methods

- ▶ Matching can easily be accomplished at one specific frequency.
- ▶ The design depends on component values or lengths
 - ▶ Then, the bandwidth is generally narrow and depends to some extent on how far apart R_o and Z_L are from each other.

Outline

Introduction

Narrow-Band Methods

Lumped Element Matching

Stub Tuners

Quarter-Wave Transformer

Varying Bandwidth Methods

Lumped Element Methods

Multiple Quarter-wave Sections

Bode-Fano Criterion


Theory of Small Reflections

Conclusions

Lumped Element Matching



- ▶ Adjusting impedances to get maximum power transfer
- ▶ Can be used at higher frequencies now due to surface-mount technology
- ▶ Component losses can limit usefulness of matching network

L-Nets: Analytic Considerations

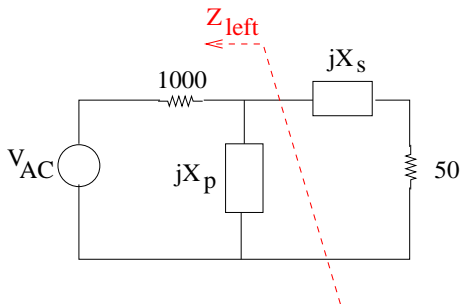

- ▶ Note how jX_p pulls $1k\Omega$ down since in parallel
- ▶ Choose X_p so that $R_{left} = 50\Omega$ (to match).
- ▶ Then, jX_s used to cancel jX_{left}

Answers to Prev. Problem

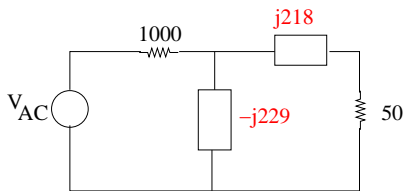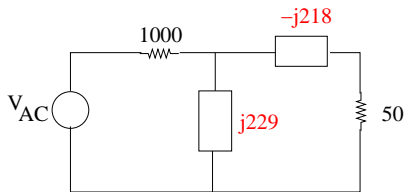

- ▶ On left, 0 output at DC
- ▶ On right, 0 output at infinite frequency

Analysis

- ▶ Let us define

$$Q_{EL} = \sqrt{\frac{R_{high}}{R_{low}} - 1}$$

- ▶ Then, we have

$$\frac{X_s}{R_{low}} = \frac{R_{high}}{X_p} = Q_{EL}$$

- ▶ However, Q_{EL} is not the $Q = f_o/\Delta f$ but it can be shown that

$$\frac{1}{Q} = \frac{2}{Q_{EL}}$$

- ▶ Note that as R_{high}/R_{low} increases, the Q increases.

L-Nets on a Smith Chart

- ▶ Need impedance Smith chart with $g = 1$ circle added
- ▶ Example
 - ▶ $Z_L = 200 - j100$, 100Ω line, $f = 500$ MHz.
 - ▶ $z_L = 2 - j1$
 - ▶ inside $r = 1$ circle \rightarrow high impedance $\rightarrow X_p$ first.
 - ▶ (see chart)

Outline

Introduction

Narrow-Band Methods

Lumped Element Matching

Stub Tuners

Quarter-Wave Transformer

Varying Bandwidth Methods

Lumped Element Methods


Multiple Quarter-wave Sections

Bode-Fano Criterion

Theory of Small Reflections

Conclusions

Single Stub Tuner

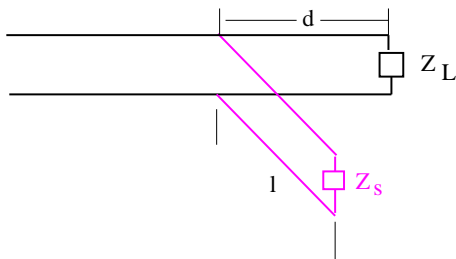

- ▶ There are two variables, d and ℓ .
- ▶ Z_S is either an open circuit or a short circuit
- ▶ The stub adds only reactance
- ▶ Principle
 - ▶ Find d so that $y_{in} = 1 \pm jx$
 - ▶ Find ℓ so that $y_{in,stub} = 1 \mp jx$

Example

- ▶ $Z_L = 60 - j80$ ($R = 60\Omega$, $C=0.995\text{pF}$ at 2 GHz)
- ▶ $Z_o = 50\Omega$
- ▶ $z_L = 1.2 - j1.6$
- ▶ see Smith chart

Outline

Introduction

Narrow-Band Methods

Lumped Element Matching

Stub Tuners

Quarter-Wave Transformer

Varying Bandwidth Methods

Lumped Element Methods

Multiple Quarter-wave Sections

Bode-Fano Criterion

Theory of Small Reflections

Conclusions

Quarter-Wave Transformer

- ▶ Recall the input impedance relation:

$$Z_{in} = R_o \frac{Z_L + jR_o \tan \beta \ell}{R_o + jZ_L \tan \beta \ell}$$

- ▶ if Z_L , R_o are real, and $\ell = \lambda/4$, then,
 $\beta \ell = (2\pi/\lambda)(\lambda/4) = \pi/2$ and $\tan(\pi/2) \rightarrow \infty$.
- ▶ Therefore,

$$Z_{in} = \frac{R_o^2}{Z_L}$$

Quarter-Wave Transformers, Part II

- ▶ Recall:

$$Z_{in} = \frac{R_o^2}{Z_L}$$

- ▶ This relationship can be used to define a section of transmission line with impedance R' which is $\lambda/4$ long and has characteristic impedance:

$$R' = \sqrt{R_o R_L}$$

and there will be no reflections at the center frequency.

Bandwidth Considerations

- ▶ In all of the methods discussed, the match is “perfect” at a single frequency.
- ▶ Sometimes, the bandwidth of the match is important.
- ▶ There are instances where a narrower bandwidth or a wider bandwidth is desired.
- ▶ For the rest of the presentation, we will investigate techniques (mostly based on previous methods) that provide either a wider or a narrower bandwidth.
- ▶ The Bode-Fano Criterion also helps us understand some of the fundamental limitations of wide-band matching networks.

Outline

Introduction

Narrow-Band Methods

Lumped Element Matching

Stub Tuners

Quarter-Wave Transformer

Varying Bandwidth Methods

Lumped Element Methods


Multiple Quarter-wave Sections

Bode-Fano Criterion

Theory of Small Reflections


Conclusions

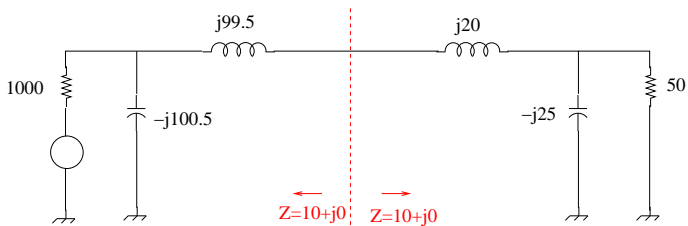Lumped Element Methods: Narrower Bandwidth



- ▶ Pi net will have narrower BW
- ▶ Intermediate impedance is additional degree of freedom
- ▶ Can also choose $Z > R_{high}$, then, L-nets flip and have T-net

Lumped Element Methods: Wider Bandwidth

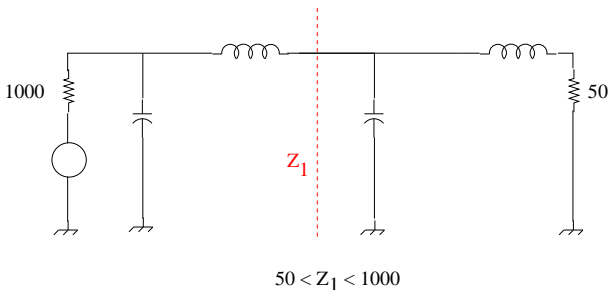

- ▶ Multiple Sections can be used
 - ▶ Many sections and structure begins to look like tapered t-line

Outline

Introduction

Narrow-Band Methods

Lumped Element Matching

Stub Tuners

Quarter-Wave Transformer

Varying Bandwidth Methods

Lumped Element Methods

Multiple Quarter-wave Sections

Bode-Fano Criterion


Theory of Small Reflections

Conclusions

Multiple Quarter-wave Section

- ▶ Can use multiple sections to create wider bandwidth match
 - ▶ Each section has length $\lambda/4$
 - ▶ Each section has impedance between R_o and R_L
- ▶ Structure will take more space (length)
- ▶ More t-line will also mean more loss in structure

Example

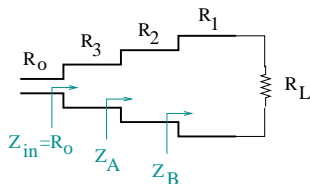

- ▶ For example, suppose have 3 sections. Let

$$r = \frac{R_L}{Z_B} = \frac{Z_B}{Z_A} = \frac{Z_A}{R_0} \quad \text{or} \quad \frac{R_L}{R_0} = \frac{Z_A}{R_0} \frac{Z_B}{Z_A} \frac{R_L}{Z_B} = r^3$$

- ▶ Therefore, use

$$r = \sqrt[3]{\frac{R_L}{R_0}}$$

Outline

Introduction

Narrow-Band Methods

 Lumped Element Matching

 Stub Tuners

 Quarter-Wave Transformer

Varying Bandwidth Methods

 Lumped Element Methods

 Multiple Quarter-wave Sections


Bode-Fano Criterion

 Theory of Small Reflections

Conclusions

Bode-Fano Criterion: Introduction

- ▶ Bode-Fano Criterion answers:
 - ▶ Can we achieve perfect match ($\Gamma = 0$) over a bandwidth (BW)?
 - ▶ If not, how well can we do?
 - ▶ What is tradeoff between $|\Gamma|$ and BW?
 - ▶ How complex must matching net be?
- ▶ Bode-Fano gives theoretical limit on $|\Gamma|_{min}$

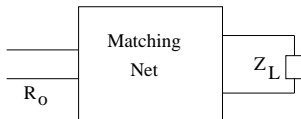

Bode-Fano Criterion

- ▶ Criterion related to


$$\int_0^{\infty} \ln \frac{1}{|\Gamma(\omega)|} d\omega$$

For example, with a parallel RC load (ICBST):

$$\int_0^{\infty} \ln \frac{1}{|\Gamma(\omega)|} d\omega \leq \frac{\pi}{RC}$$

- ▶ if $|\Gamma(\omega)| = 1$, have complete reflection and contribution to integral is zero.
- ▶ Thus, criterion is concerned with pass band

Simple Example

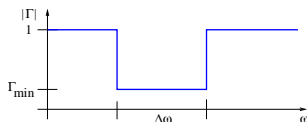

- ▶ Using $|\Gamma|$ as shown,

$$\int_0^{\infty} \ln \frac{1}{|\Gamma|} d\omega = \int_{\Delta\omega} \ln \frac{1}{\Gamma_{min}} d\omega = \Delta\omega \ln \frac{1}{\Gamma_{min}} \leq \frac{\pi}{RC}$$

- ▶ Conclusions:

- ▶ For a given load, as $\Delta\omega$ increases, Γ_{min} increases
- ▶ Γ in passband cannot be zero unless $\Delta\omega = 0$.
- ▶ as R or C increase, $\Delta\omega$ or $1/\Gamma_{min}$ must decrease (higher Q implies harder to match)

Outline

Introduction

Narrow-Band Methods

Lumped Element Matching

Stub Tuners

Quarter-Wave Transformer

Varying Bandwidth Methods

Lumped Element Methods

Multiple Quarter-wave Sections

Bode-Fano Criterion

Theory of Small Reflections

Conclusions

Conclusions

- ▶ Many methods available for impedance matching
 - ▶ narrow-band methods
 - ▶ wider-band methods
- ▶ Bode-Fano Criterion helps us understand the fundamental limits of wide-band matching
- ▶ (not covered) Theory of small reflections can be used to create filter-like designs that both match the load to the line and provide filtering.